

🔗 main ▾

...

Digital-Electronics-1 / 08-traffic_lights /



AnaSampaio13 ...

11 seconds ago ⌚

..



Pictures

8 minutes ago



README.md

11 seconds ago

☰ README.md



#Digital-Electronics-1



<https://github.com/AnaSampaio13/Digital-Electronics-1>



##Exercise 1

###State table

Input P	0	0	1	1	0	1	0	1	1	1	1	0	
Clock	↑	↑	↑	↑	↑	↑	↑	↑	↑	↑	↑	↑	
State	A	A	B	C	C	D	A	B	C	D	B	B	
Output R	0	0	0	0	0	1	0	0	0	1	0	0	

###Image

 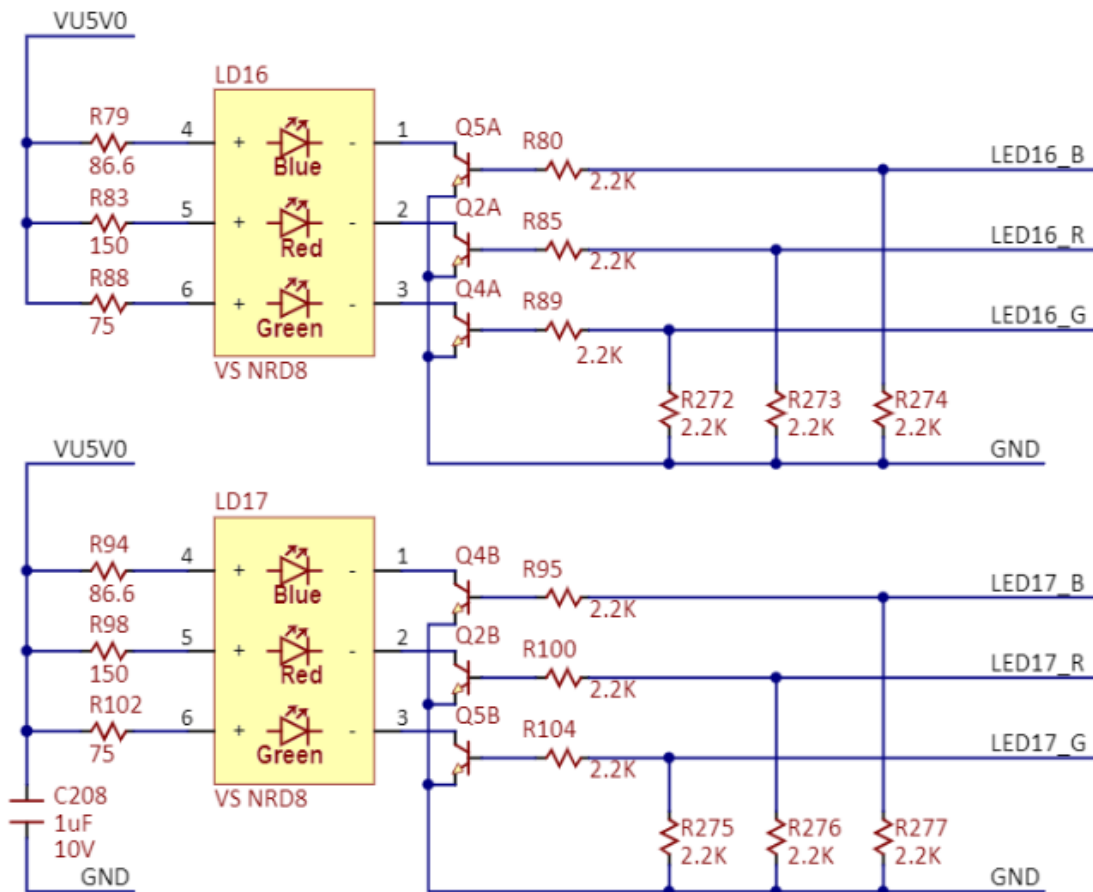


  

RGB LED	Artix-7 pin names	Red	Yellow	Green
LD16	N15, M16, R12	1,0,0	1,1,0	0,1,0
LD17	N16, R11, G14	1,0,0	1,1,0	0,1,0

##Exercise 2

###State diagram

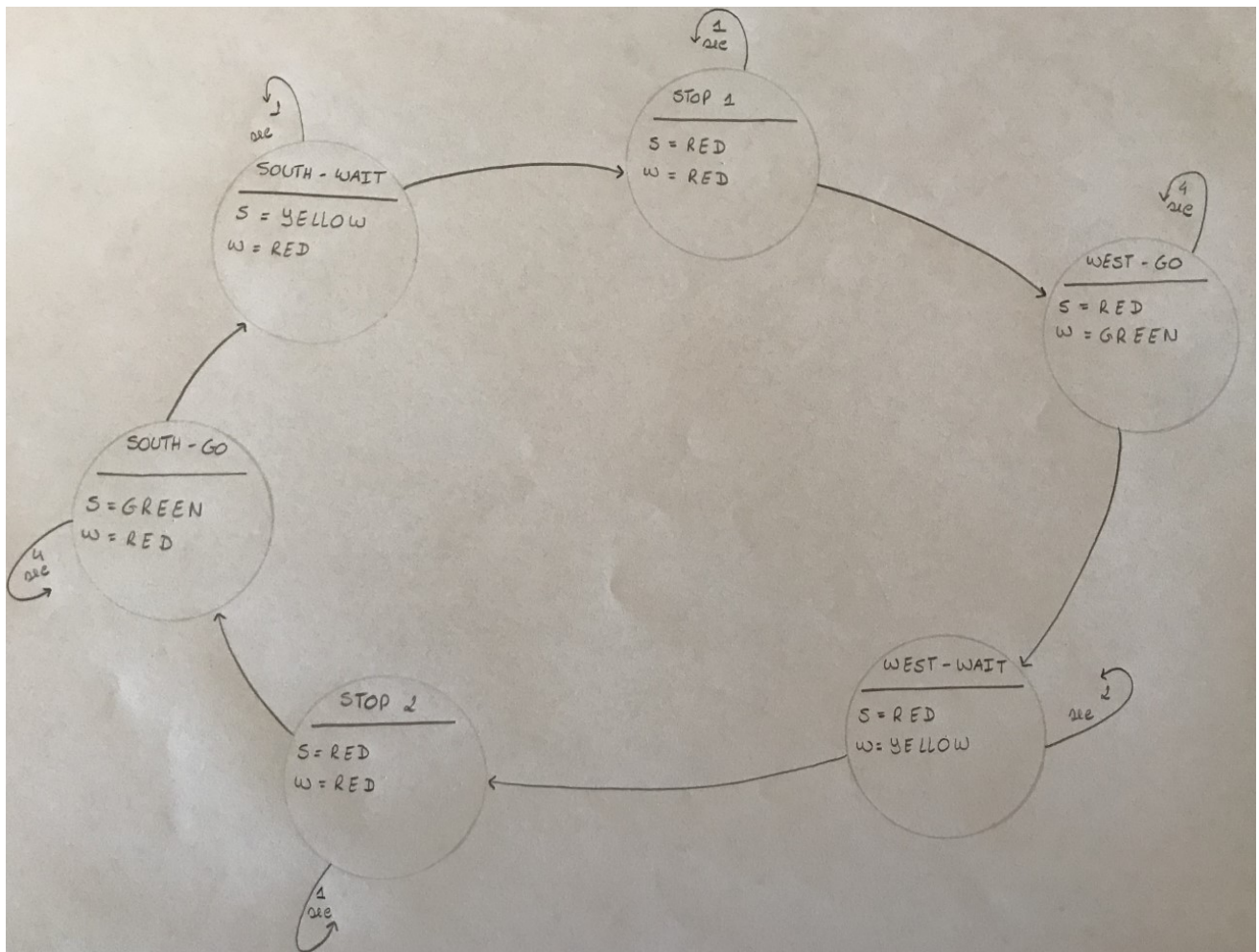

###Listing of VHDL code of sequential process

```

p_traffic_fsm : process(clk)
begin
    if rising_edge(clk) then

```

```

if (reset = '1') then          -- Synchronous reset
    s_state <= STOP1;          -- Set initial state
    s_cnt   <= c_ZERO;         -- Clear all bits
elsif (s_en = '1') then
    -- Every 250 ms, CASE checks the value of the s_state
    -- variable and changes to the next state according
    -- to the delay value.
    case s_state is
        -- If the current state is STOP1, then wait 1 sec
        -- and move to the next GO_WAIT state.
        when STOP1 =>
            -- Count up to c_DELAY_1SEC
            if (s_cnt < c_DELAY_1SEC) then
                s_cnt <= s_cnt + 1;
            else
                -- Move to the next state
                s_state <= WEST_GO;
                -- Reset local counter value
                s_cnt   <= c_ZERO;
            end if;
        when WEST_GO =>
            if (s_cnt < c_DELAY_2SEC) then
                s_cnt <= s_cnt + 1;
            else
                s_state <= WEST_WAIT;
                s_cnt   <= c_ZERO;
            end if;
        when WEST_WAIT =>
            if (s_cnt < c_DELAY_4SEC) then
                s_cnt <= s_cnt + 1;
            else
                s_state <= STOP2;
                s_cnt   <= c_ZERO;
            end if;
        when STOP2 =>
            if (s_cnt < c_DELAY_1SEC) then
                s_cnt <= s_cnt + 1;
            else
                s_state <= SOUTH_GO;
                s_cnt   <= c_ZERO;
            end if;
        when SOUTH_GO =>
            if (s_cnt < c_DELAY_2SEC) then
                s_cnt <= s_cnt + 1;
            else
                s_state <= SOUTH_WAIT;
                s_cnt   <= c_ZERO;
            end if;
        when SOUTH_WAIT =>
            if (s_cnt < c_DELAY_4SEC) then
                s_cnt <= s_cnt + 1;
            else
                s_state <= STOP1;
                s_cnt   <= c_ZERO;
            end if;
    end case;
end if;

```

```

-- It is a good programming practice to use the
-- OTHERS clause, even if all CASE choices have
-- been made.
when others =>
    s_state <= STOP1;
end case;
end if; -- Synchronous reset
end if; -- Rising edge
end process p_traffic_fsm;

```


###Listing of VHDL code of combinatorial process

```

p_output_fsm : process(s_state)
begin
    case s_state is
        when STOP1 =>
            south_o <= "100"; -- Red
            west_o  <= "100"; -- Red
        when WEST_GO =>
            south_o <= "100"; -- Red
            west_o  <= "010"; -- Green
        when WEST_WAIT =>
            south_o <= "100"; -- Red
            west_o  <= "110"; -- Yellow
        when STOP2 =>
            south_o <= "100"; -- Red
            west_o  <= "100"; -- Red
        when SOUTH_GO =>
            south_o <= "010"; -- Green
            west_o  <= "100"; -- Red
        when SOUTH_WAIT =>
            south_o <= "110"; -- Yellow
            west_o  <= "100"; -- Red
        when others =>
            south_o <= "100"; -- Red
            west_o  <= "100"; -- Red
    end case;
end process p_output_fsm;

```

###Screenshot

 


##Exercise 3

###State table

Input	No bikes	West_i	West_i	No bikes	South_i	South_i
Delay	4 seconds	1 second	4 seconds	4 seconds	4 seconds	1 second
State	South_go	South_wait	West_go	West_go	West_go	West_wait
Output	S: Green; W: Red	S: Yellow; W: Red	S: Red; W: Green	S: Red; W: Green	S: Red; W: Green	S: Red; W: Yellow

###State diagram

 

###Listing of VHDL code of sequential process

```
p_smart_traffic_fsm : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then          -- Synchronous reset
            s_state <= STOP1 ;          -- Set initial state
            s_cnt   <= c_ZERO;          -- Clear all bits
        elsif (s_en = '1') then
            -- Every 250 ms, CASE checks the value of the s_state
            -- variable and changes to the next state according
            -- to the delay value.
            case s_state is
                when South_go =>
                    -- Count up to c_DELAY_4SEC
                    if (s_cnt < c_DELAY_4SEC) then
                        s_cnt <= s_cnt + 1;
                    elsif (west_i = '1') then
                        -- Move to the next state
                        s_state <= South_wait;
                        -- Reset local counter value
                        s_cnt   <= c_ZERO;
                    end if;
                when South_wait =>
                    -- Count up to c_DELAY_1SEC
                    if (s_cnt < c_DELAY_1SEC) then
                        s_cnt <= s_cnt + 1;
                    else
                        -- Move to the next state
                        s_state <= West_go;
                        -- Reset local counter value
                        s_cnt   <= c_ZERO;
                    end if;
                when West_go =>
                    -- Count up to c_DELAY_4SEC
                    if (s_cnt < c_DELAY_4SEC) then
                        s_cnt <= s_cnt + 1;
                    elsif (South_i = '1') then
                        -- Move to the next state
                        s_state <= West_wait;
                        -- Reset local counter value
                        s_cnt   <= c_ZERO;
                    end if;
                when West_wait =>
                    -- Count up to c_DELAY_1SEC
                    if (s_cnt < c_DELAY_1SEC) then
                        s_cnt <= s_cnt + 1;
                    else
                        -- Move to the next state
                        s_state <= South_go;
                        -- Reset local counter value
                        s_cnt   <= c_ZERO;
                    end if;
            end case;
            -- It is a good programming practice to use the
```



```
-- OTHERS clause, even if all CASE choices have
-- been made.
when others =>
    s_state <= South_go;
end case;
end if; -- Synchronous reset
end if; -- Rising edge
end process p_smart_traffic_fsm;
```
