



Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

[Read the guide](#)

 [AnaSampaio13](#) / [Digital-Electronics-1](#)

 MIT License

☆ 0 stars 🍴 0 forks

☆ Star

👁 Unwatch ▼

Code

Issues 2

Pull requests

Actions

Projects

Wiki

Security

Insights

Settings

🔗 main ▼



AnaSampaio13 ...

26 seconds ago



[View code](#)

README.md



Digital-Electronics-1

<https://github.com/AnaSampaio13/Digital-Electronics-1>

🔗 Exercise 1

```
-----  
--  
-- Example of basic OR, AND, XOR gates.
```

```

-- Nexys A7-50T, Vivado v2020.1, EDA Playground
--
-- Copyright (c) 2019-2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;           -- Standard library
use ieee.std_logic_1164.all; -- Package for data types and logic operations

-----

-- Entity declaration for basic gates
-----
entity gates is
    port(
        a_i    : in  std_logic;    -- Data input
        b_i    : in  std_logic;    -- Data input
        c_i    : in  std_logic;    -- Data input
        f_base  : out std_logic;    -- Output function
        f_nand  : out std_logic;    -- Output function
        f_nor   : out std_logic;    -- Output function
    );
end entity gates;

-----

-- Architecture body for basic gates
-----
architecture dataflow of gates is
begin
    f_base <= ((not b_i) and a_i) or ((not c_i) and (not b_i));
    f_nand <= ((not b_i) nand a_i) nand ((not c_i) nand (not b_i));
    f_nor  <= ((not b_i) nor a_i) nor ((not c_i) nor b_i);

end architecture dataflow;

-----

--
-- Testbench for basic gates circuit.
-- Nexys A7-50T, Vivado v2020.1, EDA Playground
--
-- Copyright (c) 2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;
use ieee.std_logic_1164.all;

-----

-- Entity declaration for testbench

```

```

-----
entity tb_gates is
    -- Entity of testbench is always empty
end entity tb_gates;

-----

-- Architecture body for testbench
-----

architecture testbench of tb_gates is

    -- Local signals
    signal s_a      : std_logic;
    signal s_b      : std_logic;
    signal s_c      : std_logic;
    signal s_d      : std_logic;
    signal s_e      : std_logic;
    signal s_f      : std_logic;

begin

    -- Connecting testbench signals with gates entity (Unit Under Test)
    uut_gates : entity work.gates
        port map(
            a_i    => s_a,
            b_i    => s_b,
            c_i    => s_c,
            f_base => s_d,
            f_nand => s_e,
            f_nor  => s_f

        );

    -----

    -- Data generation process
    -----

    p_stimulus : process
    begin
        s_b <= '0';           -- Set input values and wait for 100 ns
        s_a <= '0';
        s_c <= '0';
        wait for 100 ns;
        s_c <= '0';
        s_b <= '0';
        s_a <= '1';
        wait for 100 ns;
        s_c <= '0';
        s_b <= '1';
        s_a <= '0';
        wait for 100 ns;
        s_c <= '0';
        s_b <= '1';
        s_a <= '1';
        wait for 100 ns;
        s_c <= '1';
        s_b <= '0';
    end process;
end architecture testbench;

```


```

s_a <= '0';
wait for 100 ns;
s_c <= '1';
s_b <= '0';
s_a <= '1';
wait for 100 ns;
s_c <= '1';
s_b <= '1';
s_a <= '0';
wait for 100 ns;
s_c <= '1';
s_b <= '1';
s_a <= '1';
wait; -- Process is suspended forever
end process p_stimulus;

end architecture testbench;

```

Waveform #Exercise 1:

 

EDA Playground Example

Exercise 2

```

-----
--
-- Example of basic OR, AND, XOR gates.
-- Nexys A7-50T, Vivado v2020.1, EDA Playground
--
-- Copyright (c) 2019-2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee; -- Standard library
use ieee.std_logic_1164.all; -- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----

entity gates is
    port(

```

```

    x_i    : in  std_logic;      -- Data input
    y_i    : in  std_logic;      -- Data input
    z_i    : in  std_logic;      -- Data input
    fres_1 : out std_logic;
    fres_2 : out std_logic;
    fres_3 : out std_logic;
    fres_4 : out std_logic

);
end entity gates;

-----
-- Architecture body for basic gates
-----
architecture dataflow of gates is
begin
    fres_1 <= (x_i and y_i) or (x_i and z_i);
    fres_2 <= x_i and (y_i or z_i);
    fres_3 <= (x_i or y_i) and (x_i or z_i) ;
    fres_4 <= x_i or (y_i and z_i);

end architecture dataflow;

-----
--
-- Testbench for basic gates circuit.
-- Nexys A7-50T, Vivado v2020.1, EDA Playground
--
-- Copyright (c) 2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----
entity tb_gates is
    -- Entity of testbench is always empty
end entity tb_gates;

-----
-- Architecture body for testbench
-----
architecture testbench of tb_gates is

    -- Local signals
    signal s_x    : std_logic;
    signal s_y    : std_logic;

```

```

signal s_z      : std_logic;
signal s_fres1   : std_logic;
signal s_fres2   : std_logic;
signal s_fres3   : std_logic;
signal s_fres4   : std_logic;

begin
  -- Connecting testbench signals with gates entity (Unit Under Test)
  uut_gates : entity work.gates
    port map(
      x_i      => s_x,
      y_i      => s_y,
      z_i      => s_z,
      fres_1   => s_fres1,
      fres_2   => s_fres2,
      fres_3   => s_fres3,
      fres_4   => s_fres4

    );


  -----
  -- Data generation process
  -----

  p_stimulus : process
  begin
    s_y <= '0';          -- Set input values and wait for 100 ns
    s_x <= '0';
    s_z <= '0';
    wait for 100 ns;
    s_z <= '0';
    s_y <= '0';
    s_x <= '1';
    wait for 100 ns;
    s_z <= '0';
    s_y <= '1';
    s_x <= '0';
    wait for 100 ns;
    s_z <= '0';
    s_y <= '1';
    s_x <= '1';
    wait for 100 ns;
    s_z <= '1';
    s_y <= '0';
    s_x <= '0';
    wait for 100 ns;
    s_z <= '1';
    s_y <= '0';
    s_x <= '1';
    wait for 100 ns;
    s_z <= '1';
    s_y <= '1';
    s_x <= '0';
    wait for 100 ns;
    s_z <= '1';
    s_y <= '1';
  end process;

```

```
s_x <= '1';  
wait; -- Process is suspended forever  
end process p_stimulus;  
  
end architecture testbench;
```

Waveform #Exercise 2:

 

EDA Playground Example

Releases

No releases published
[Create a new release](#)

Packages

No packages published
[Publish your first package](#)